

ELEC2146

Electrical Engineering Modelling and Simulation

Transfer Functions


Dr Ray Eaton

S2, 2016

Overview

- System representations
- Transfer functions
 - Converting to/from differential equations
- Magnitude responses
- Pole-zero diagrams
- Putting it all together

System Representations

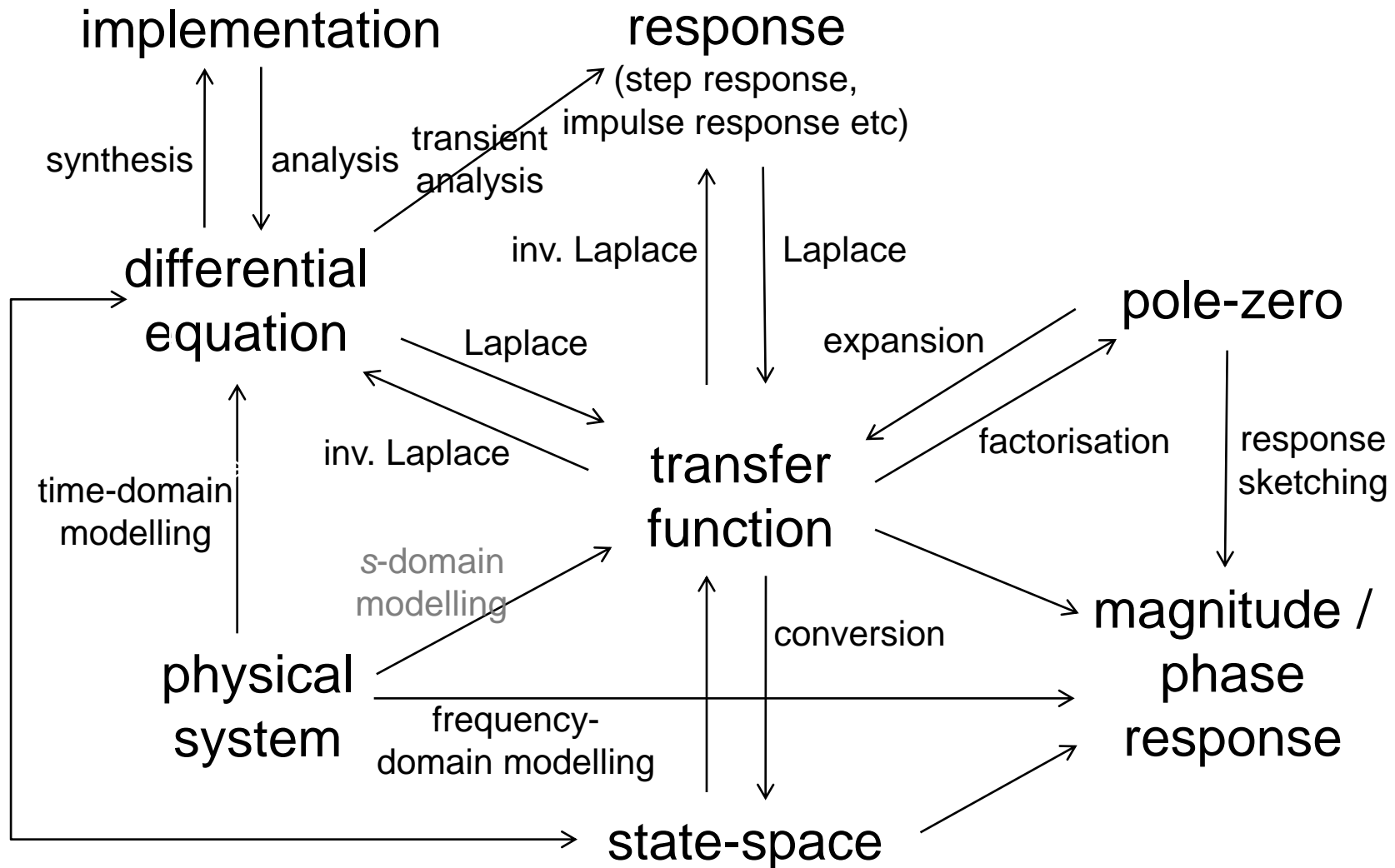

Transfer Functions

- A general linear, time-invariant continuous system can be written as

$$y(t) = b_M \frac{d^M x}{dt^M} + \dots + b_1 \frac{dx}{dt} + b_0 x(t) - a_N \frac{d^N y}{dt^N} - \dots - a_1 \frac{dy}{dt}$$

- Take Laplace transform:

$$Y(s) = b_M s^M X(s) + \dots + b_1 s X(s) + b_0 X(s) - a_N s^N Y(s) - \dots - a_1 s Y(s)$$

- Transfer function:

$$H(s) = \frac{Y(s)}{X(s)}$$


Transfer Functions

$$H(s) = \frac{b_M s^M + \dots + b_1 s + b_0}{a_N s^N + \dots + a_1 s + a_0}$$

- Completely specifies behaviour of system in response to any input
 - A property of the *circuit/system only*
 - Obtained for the case of zero initial conditions
 - A rational function of polynomials in s
- Since $Y(s) = H(s)X(s)$, the transfer function is a path to determining the response to a given input

Transfer Functions

- Example:

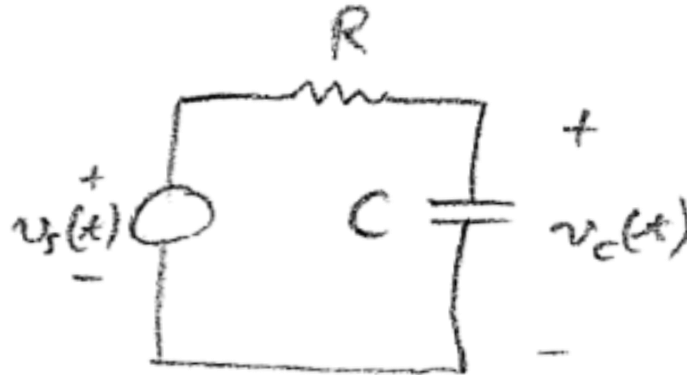

- To obtain transfer function, either analyse in time domain and take Laplace transform

$$v_s(t) - v_c(t) = RC \frac{dv_c(t)}{dt} \quad v_c(t) + RC \frac{dv_c(t)}{dt} = v_s(t)$$

$$\Leftrightarrow V_C(s) + sRCV_C(s) = V_S(s)$$

$$H(s) = \frac{V_C(s)}{V_S(s)} = \frac{1}{RCs + 1}$$

Transfer Functions

- OR: Analyse in s-domain and take Laplace transform

$$V_s(s) = \frac{1}{sC} I(s) + RI(s)$$

$$I(s) = sCV_C(s)$$

$$V_s(s) = \frac{1}{sC} sCV_C(s) + RsCV_C(s)$$

$$H(s) = \frac{V_C(s)}{V_s(s)} = \frac{1}{RCs + 1}$$

Transfer Functions

- Determine response $v_C(t)$ to $v_s(t) = e^{-2000t}u(t)$ if $R = 1 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$

$$V_s(s) = H(s)V_C(s) = \frac{1}{0.001s + 1} \frac{1}{s + 2000}$$

$$= 1000 \left(\frac{\frac{1}{1000}}{s + 1000} - \frac{\frac{1}{1000}}{s + 2000} \right)$$

$$\Leftrightarrow v_s(t) = (e^{-1000t} - e^{-2000t})u(t)$$


Frequency Response

- The transfer function allows determination of the frequency response

$$H(j\omega) = H(s) \Big|_{s=j\omega}$$

– What is $s = j\omega$?

- An axis of the s-plane

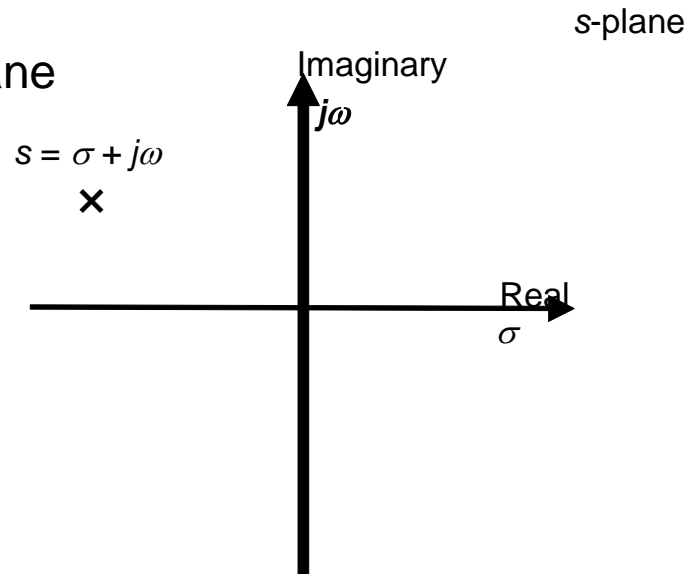

Frequency Response

- Two quantities are of interest:

- Magnitude $|H(j\omega)|$

- Phase $\phi(H(j\omega))$

- Example: $H(s) = \frac{1}{RCs + 1}$

$$H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$|H(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{\omega^2 R^2 C^2 + 1}}$$

$$\phi(H(j\omega)) = \phi\left(\frac{1}{j\omega RC + 1}\right) = -\tan^{-1}(\omega RC)$$

Poles and Zeroes

- In this course, all transfer function polynomial coefficients are real
 - Derived from real systems, or models of real systems
 - Roots of the numerator and denominator polynomials are either real or occur in complex conjugate pairs
- Roots of the numerator polynomial are referred to as zeroes
- Roots of the denominator polynomial are referred to as poles

Poles and Zeroes

- Require factorisation of the numerator and denominator

$$H(s) = \frac{b_M s^M + \dots + b_1 s + b_0}{a_N s^N + \dots + a_1 s + a_0}$$

$$= \frac{b_M (s - z_1)(s - z_2) \dots (s - z_M)}{a_N (s - p_1)(s - p_2) \dots (s - p_N)}$$

Diagram illustrating the factorization of the transfer function $H(s)$ into its poles and zeroes form. The numerator is factored into a gain term b_M and a product of zero terms $(s - z_1)(s - z_2) \dots (s - z_M)$. The denominator is factored into a product of pole terms $(s - p_1)(s - p_2) \dots (s - p_N)$. The gain term b_M is circled in red and labeled "gain term". The zero terms are labeled "zeroes" and the pole terms are labeled "poles".

Poles and Zeroes

- A system can be completely characterised by its poles and zeroes
 - Together with a gain term
- Why represent a system in terms of poles and zeroes ?
 - Conveys a lot of understanding visually
 - Gives idea of the frequency response
 - Including for more complex, higher-order systems
 - Can see system stability
 - Used in control systems analysis/design


Poles and Zeroes

- Pole-zero plotting conventions
 - Zeros are represented using a circle ○
 - Poles are represented using a cross ×

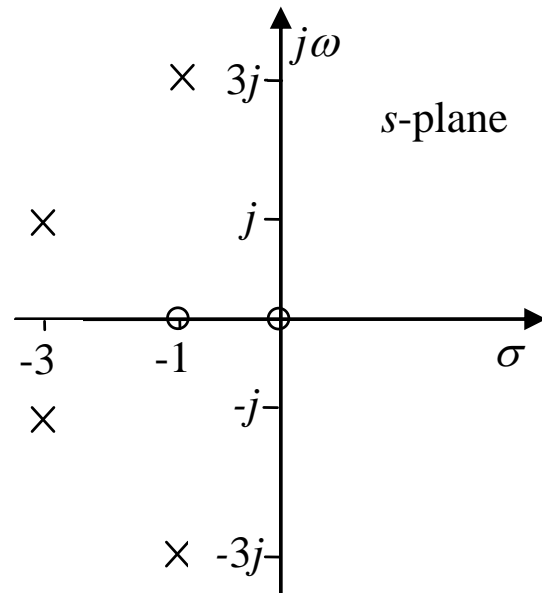- Example:

$$H(s) = \frac{s^2 + s}{s^4 + 8s^3 + 32s^2 + 80s + 100}$$


- Zeros at $s = 0, -1$
- Poles at $s = -1 \pm 3j, -3 \pm j$



Poles and Zeroes


■ Relationship to magnitude response

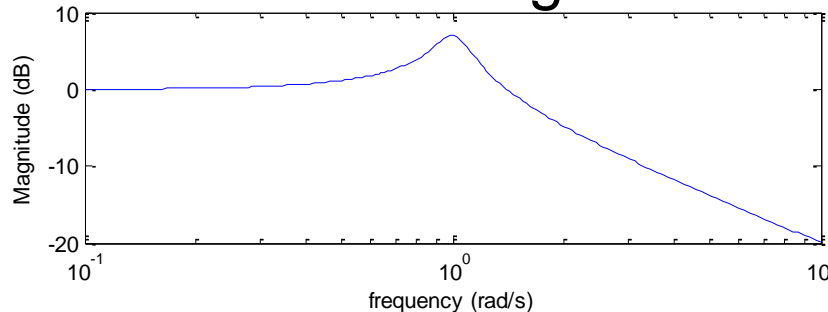- A pole close to the $j\omega$ axis at frequency ω will produce a strong, narrow peak at ω , followed by a 20 dB/dec decrease in magnitude response



$$-0.1 \pm j$$

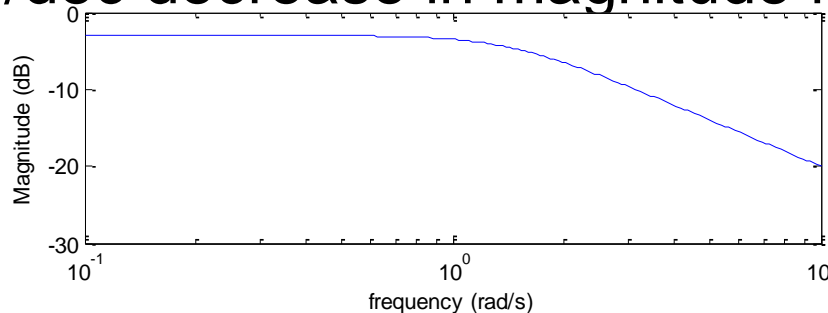- A pole far from the $j\omega$ axis at frequency ω will produce a very slight, broad peak at ω , followed by a 20 dB/dec decrease in magnitude response




$$-1 \pm j$$

Poles and Zeroes


■ Relationship to magnitude response

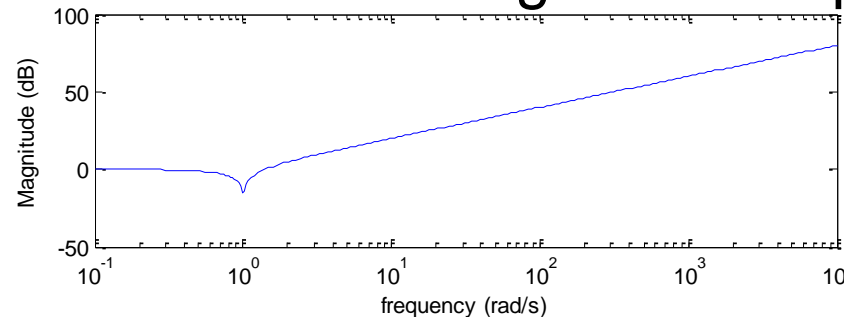- A zero close to the $j\omega$ axis at frequency ω will produce a strong, narrow valley at ω , followed by a 20 dB/dec increase in magnitude response



$$-0.01 \pm j$$

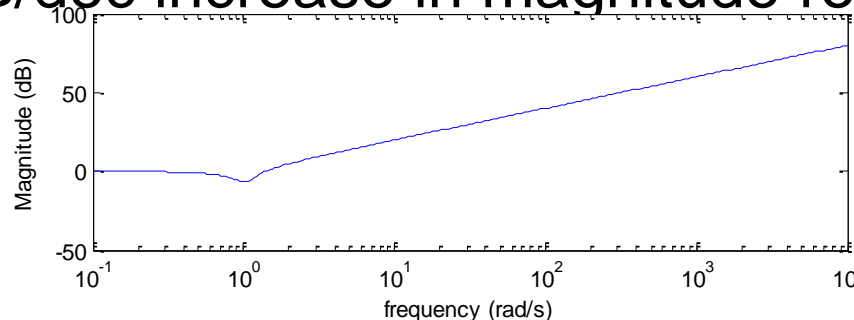
- A zero far from the $j\omega$ axis at frequency ω will produce a very slight, broad valley at ω , followed by a 20 dB/dec increase in magnitude response



$$-0.1 \pm j$$

Poles and Zeroes

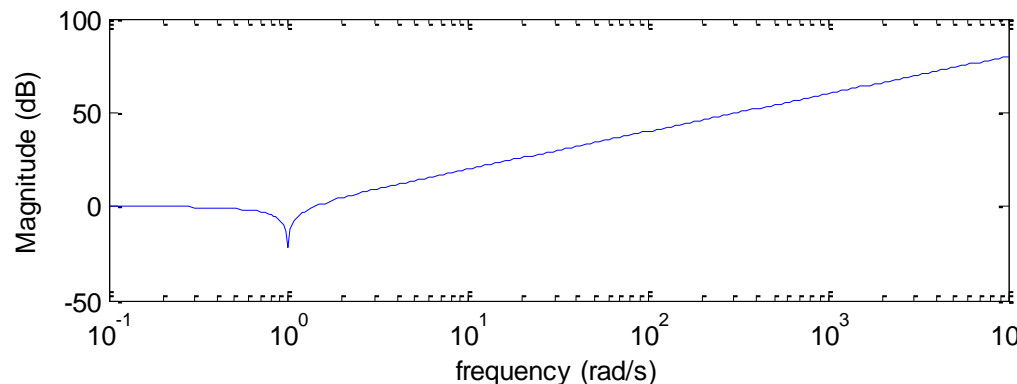- Relationship to magnitude response
 - A zero exactly on the $j\omega$ axis at frequency ω will produce a zero in the magnitude response at ω , i.e. an input signal at frequency ω will produce no output.




- Note that pole and zero locations have an impact on the phase response also, however this is not discussed in this course.

Frequency Response

- Magnitude response sketching
 - See circuit analysis text on Bode plots
 - See example in lecture notes

- Example: $H(j\omega) = \frac{1}{j\omega RC + 1}$

- Pole at $s = -\frac{1}{RC}$

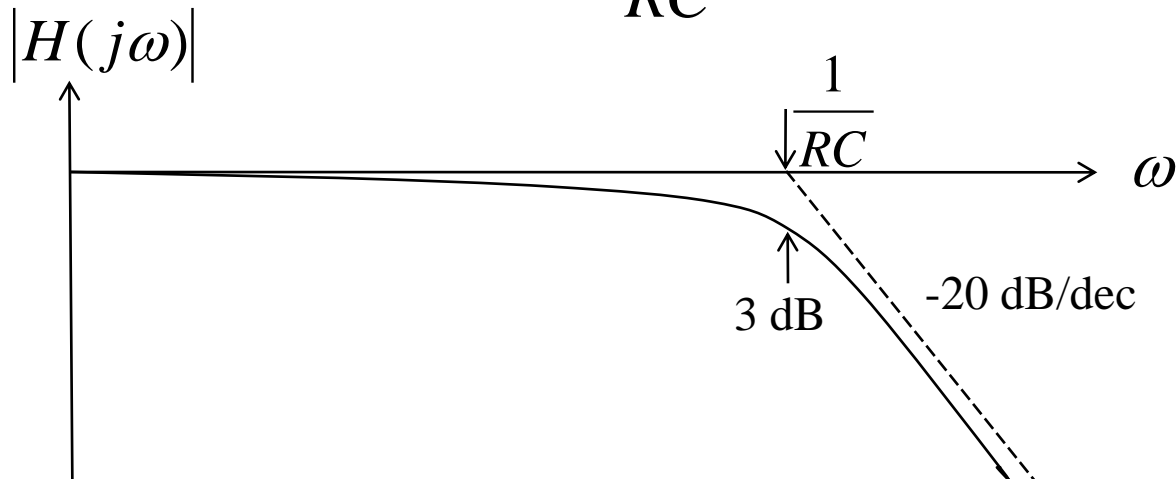


Note: pole at $-1/RC$ is on real axis, i.e. at $\omega = 0$. $\omega = RC$ is the “corner frequency” or 3 dB point. There is no peak at this frequency due to the pole; this is just the point at which the 20 dB/dec drop starts. The peak is really at $\omega = 0$ (try for example in MATLAB a very small RC (pole close to $j\omega$ axis) plotted on a linear magnitude scale)

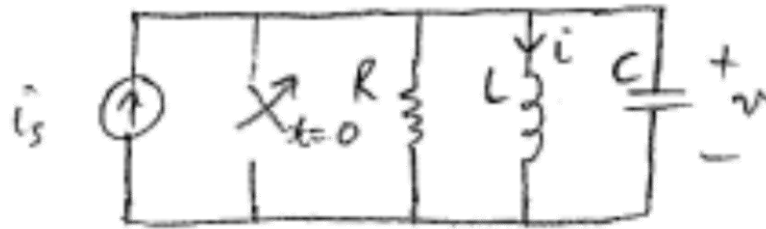Examples on previous 3 slides are for two complex conjugate poles; for single real pole responses, see any text on Bode plot sketching

One More Example

- Parallel RLC circuit
 - $R = 1 \text{ k}\Omega$, $L = 1 \text{ mH}$, $C = 1 \text{ }\mu\text{F}$



$$i_s = \frac{v}{R} + i + C \frac{dv}{dt}$$

$$\frac{1}{R} L \frac{di}{dt} + i + C \frac{d}{dt} \left(L \frac{di}{dt} \right) = i_s$$

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = \frac{1}{LC} i_s$$

One More Example

$$\frac{d^2 i}{dt^2} + 10^3 \frac{di}{dt} + 10^9 i = 10^9 i_s$$

$$a_1 = 10^3 \quad \alpha = 500$$

$$a_0 = 10^9 \quad \omega_n = \sqrt{10} \cdot 10^4$$

- Very underdamped
- Find transfer function $H(s) = \frac{I(s)}{I_s(s)}$

$$\Leftrightarrow s^2 I(s) + 10^3 s I(s) + 10^9 I(s) = 10^9 I_s(s)$$


$$H(s) = \frac{I(s)}{I_s(s)} = \frac{10^9}{s^2 + 10^3 s + 10^9}$$

One More Example

– Pole-zero diagram:

- Two poles at

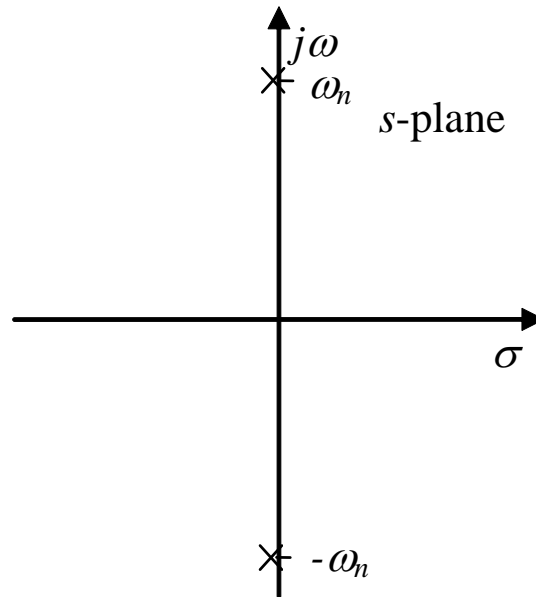
$$-500 \pm j0.9999 \cdot \sqrt{10} \cdot 10^4 \approx -500 \pm j\sqrt{10} \cdot 10^4$$



One More Example

- Magnitude response
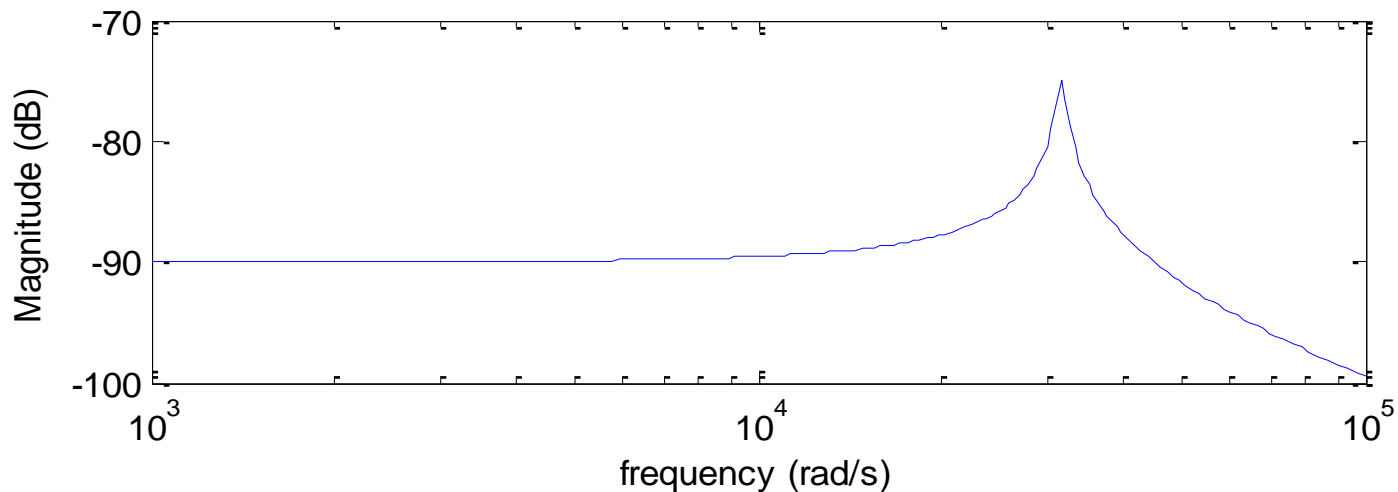
$$H(j\omega) = \frac{10^9}{\sqrt{(10^9 - \omega^2)^2 + 10^6 \omega^2}}$$




One More Example

- Impulse response

$$\begin{aligned} H(s) &= \frac{I(s)}{I_s(s)} = \frac{10^9}{s^2 + 10^3 s + 10^9} \\ &= \frac{10^9}{(s + 500)^2 + (10^9 - 0.25 \cdot 10^6)} \end{aligned}$$
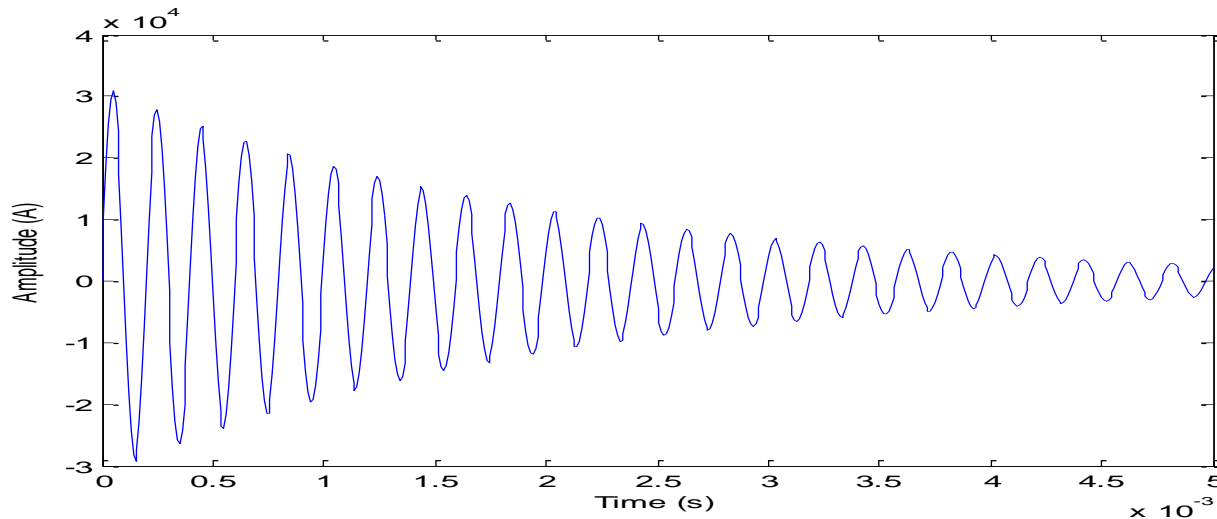
$$\leftrightarrow i(t) = h(t) \approx \sqrt{10} \cdot 10^4 e^{-500t} \sin(\sqrt{10} \cdot 10^4 t) u(t)$$



One More Example

- Step response

$$\begin{aligned} I(s) = H(s)I_s(s) &= \frac{10^9}{s^2 + 10^3 s + 10^9} \frac{1}{s} \\ &= \frac{10^9}{(s + 500)^2 + (10^9 - 0.25 \cdot 10^6)} \frac{1}{s} \end{aligned}$$

$$\begin{aligned} \Leftrightarrow i(t) &\approx \int_0^t \sqrt{10} \cdot 10^4 e^{-500\tau} \sin(\sqrt{10} \cdot 10^4 \tau) u(\tau) d\tau \\ &= -e^{-500t} \cos(\sqrt{10} \cdot 10^4 t) \Big|_0^t \\ &= 1 - e^{-500t} \cos(\sqrt{10} \cdot 10^4 t) \end{aligned}$$